

Program: BE Electrical Engineering

Curriculum Scheme: Revised 2016

Examination: Final Year Semester VII

Course Code: EEC703 and Course Name: High Voltage Direct Current Transmission

Time: 1hour

Max. Marks: 50

=====

Note to the students:- All the Questions are compulsory and carry equal marks .

Q1.	Converters used HVDC for Conversion are?
Option A:	Dynamic
Option B:	Rotating
Option C:	Static
Option D:	Moving Iron
Q2.	For Bulk power transmission over long distance HCDCT lines are preferred, on account of
Option A:	Low cost of HVDC terminals
Option B:	No harmonics problem
Option C:	minimum line power losses
Option D:	simple protection
Q3.	The longest existing HVDC link in the world is at
Option A:	UK
Option B:	USA
Option C:	Sweden
Option D:	China
Q4.	In ideal commutation process angle alpha is
Option A:	30
Option B:	90
Option C:	120
Option D:	0
Q5.	$P_d = V_d I_d$ is the DC power at
Option A:	Rectifier end
Option B:	Inverter end
Option C:	Middle of DC line
Option D:	Transformer side
Q6.	The difference between the highest and the lowest values of the output waveform is
Option A:	Peak inverse voltage

Option B:	peak to peak ripple
Option C:	Volt ampere rating
Option D:	Pulse number
Q7.	Which is incorrect conducting sequence of valves in 6-pulse converter
Option A:	6,1
Option B:	6,4
Option C:	2,3
Option D:	1,2
Q8.	Quadri valve arrangement in converter has valves in a group
Option A:	1 valve
Option B:	2 valves
Option C:	4 valves
Option D:	6 valves
Q9.	In a twelve pulse converter, valve connected in each phase are
Option A:	1
Option B:	2
Option C:	3
Option D:	4
Q10.	In converter, Overlap of currents is introduced by
Option A:	Source reactance
Option B:	Phase reactance
Option C:	Commutation capacitance
Option D:	Valve conducting
Q11.	Following transformers combination is used in HVDC Transmission
Option A:	Star-Star/Star-Delta
Option B:	Star-Star/Star-Star
Option C:	Star-Delta/Star-Star
Option D:	Delta-Star/Star-Delta
Q12.	Pole protection, DC line protection is controlled by ___ unit
Option A:	Master unit control
Option B:	System control
Option C:	VGC
Option D:	Pole unit control
Q13.	If AC voltage decreases slightly the inverter operates at
Option A:	Constant current control
Option B:	Minimum α control
Option C:	Minimum γ control
Option D:	Constant γ control

Q14.	What are the parameters to change current and power transfer in the DC link? I) Control angle of rectifier α II) Control angle of inverter β III) Tap changer on rectifier side
Option A:	I alone
Option B:	I,II and III
Option C:	I and II
Option D:	II and III
Q15.	The steady state current I_d in DC link is obtained as
Option A:	$(E_{di}-E_{dr}) / (R_{cr}+R_d-R_{ci})$
Option B:	$(E_{di}-E_{dr}) / (R_{cr}-R_d+R_{ci})$
Option C:	$(E_{dr}-E_{di}) / (R_{cr}+R_d-R_{ci})$
Option D:	$(E_{di}-E_{dr}) / (R_{cr}+R_d+R_{ci})$
Q16.	Fault on two terminal DC power link is removed by
Option A:	Breaker on DC side
Option B:	Breaker on AC side
Option C:	Current control of converter
Option D:	both a and b
Q17.	During commutation in a converter,
Option A:	No current transferred from one valve to other
Option B:	current is transferred from one valve to the other
Option C:	voltage is transferred from one valve to the other
Option D:	Converts AC to DC
Q18.	In order to satisfy basic requirements for better voltage regulation and current regulation it is always advisable to assign these parameters for the converters. Under normal operations Rectifier will take care of _____ the Inverter will take care of _____
Option A:	voltage,current
Option B:	power, voltage
Option C:	current, power
Option D:	current, voltage.
Q19.	shutting down the HVDC link means
Option A:	energization of a Bridge
Option B:	Deenergization of a Bridge
Option C:	Turning of the valves
Option D:	Turning on the valves
Q20.	In an inverter, the direct voltage across the bypass valve is normally
Option A:	Positive
Option B:	Negative
Option C:	Zero

Option D:	Infinite
Q21.	The harmonics produced under balanced conditions are known as
Option A:	AC harmonics
Option B:	DC harmonics
Option C:	Non- Characteristic Harmonics
Option D:	Characteristic Harmonics
Q22.	Ripple current is less for higher values of the
Option A:	Commutating Inductance
Option B:	DC Reactor
Option C:	Converter Transformer
Option D:	Rating of thyristor valve
Q23.	Failure to ignite inspite of positive grid and anode voltages is
Option A:	arcback
Option B:	arcthrough
Option C:	misfire
Option D:	commutation failure
Q24.	DC Reactor is used on a DC line to diminish
Option A:	DC Harmonics
Option B:	AC Harmonics
Option C:	Short Circuits
Option D:	commutation failure
Q25.	This is a self clearing fault
Option A:	Overshoots
Option B:	Commutation Failure
Option C:	Shortcircuits
Option D:	Overloads

Program: BE Electrical Engineering

Curriculum Scheme: Revised 2016

Examination: Final Year Semester VII

Course Code: EEC703 and Course Name: High Voltage Direct Current Transmission

Time: 1hour

Max. Marks: 50

=====

Question	Correct Option (Enter either 'A' or 'B' or 'C' or 'D')
Q1.	C
Q2.	C
Q3.	C
Q4	D
Q5	B
Q6	B
Q7	B
Q8.	C
Q9.	B
Q10.	A
Q11.	A
Q12.	D
Q13.	C
Q14.	B
Q15.	C
Q16.	C

Q17.	B
Q18.	D
Q19.	B
Q20.	A
Q21.	D
Q22.	B
Q23.	C
Q24.	A
Q25.	B