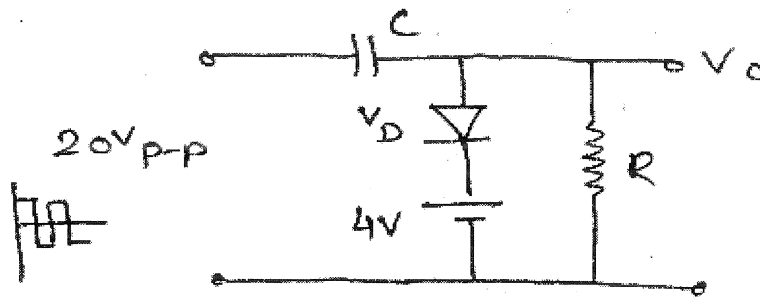


- N.B :**
1. Question No. 1 is **compulsory**.
 2. Attempt any **three** questions out of remaining **five** questions.
 3. Assume suitable data if necessary.


1. (a) Explain working of BJT as a switch. 5
- (b) Explain why FET is called as voltage controlled device. 5
- (c) Compare D-MOSFET and E-MOSFET. 5
- (d) Draw High frequency BJT and FET equivalent model. 5

2. (a) Explain zero temperature drift in FET. 5
- (b) For the following circuit, draw the output waveform. $V_D = 0.5V$ 5



- (c) For the following circuit, $V_{cc} = 15V$. Calculate 10
 - (i) Q-point
 - (ii) A_v
 - (iii) Z_i
 - (iv) Z_o

Given : $\beta = 90$

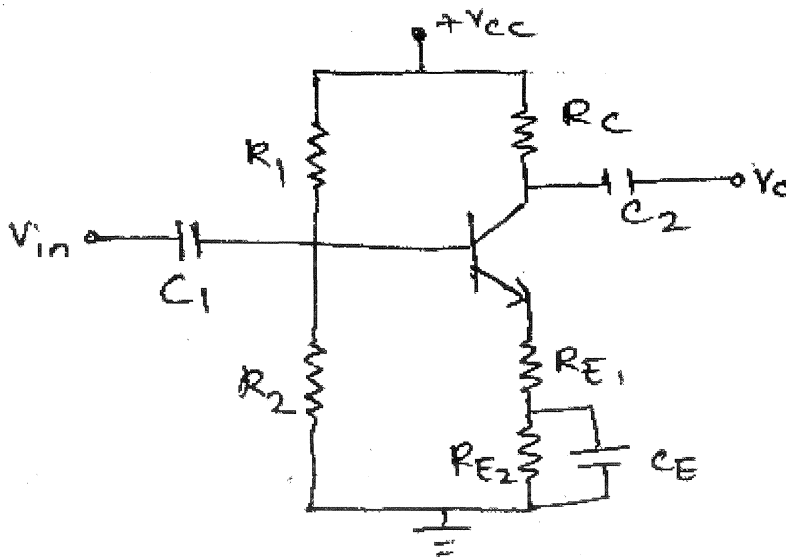

Given $R_1 = 56 K\Omega$, $R_2 = 8.2 K\Omega$, $R_{E1} = R_{E2} = 750 \Omega$
 $R_C = 6.8 K\Omega$, $C_1 = 1 \mu F$, $C_2 = 10 \mu F$, $C_E = 47 \mu F$

[TURN OVER

3. (a) Design a single state RC coupled CE Amplifier to meet the following specifications. 16
Use BC147B.
 $|A_v| \geq 150$, $f_L = 20$ Hz, $S \leq 10$, V_o (rms) = 3V
- (b) For the above design circuit calculate A_v , Z_i and Z_o . 4
4. (a) Draw a neat diagram of JFET CG amplifier and derive expression for A_v , Z_i , Z_o . 10
(b) Discuss Darlington amplifier with circuit diagram, DC and AC analysis, 10
Advantages, disadvantages and its applications.
5. (a) For the following circuit, calculate following parameters. 20
(i) Q-point for BJT and FET
(ii) Input impedance
(iii) Output impedance
(iv) Mid-frequency voltage gain (with and without load)
(v) Lower cut-off frequency.

Given : For JFET,

$$I_{DSS} = 1.6 \text{ mA}$$


$$V_p = -2 \text{ V}$$

$$V_{GSQ} = -1.5 \text{ V}$$

For BJT

$$h_{ie} = 2.7 \text{ k}\Omega$$

$$h_{fe} = 90$$

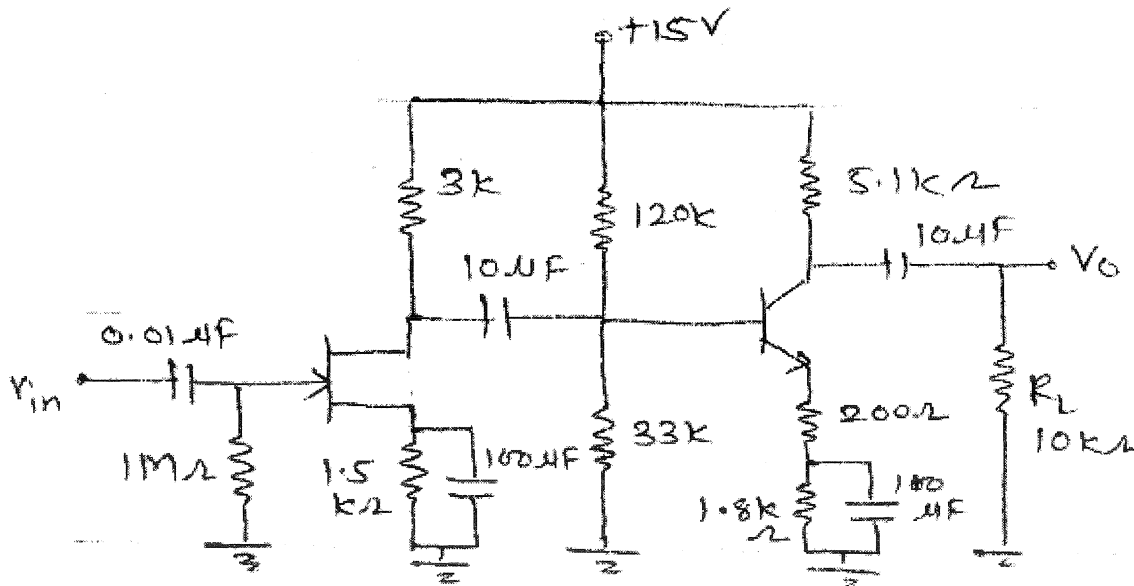


[TURN OVER

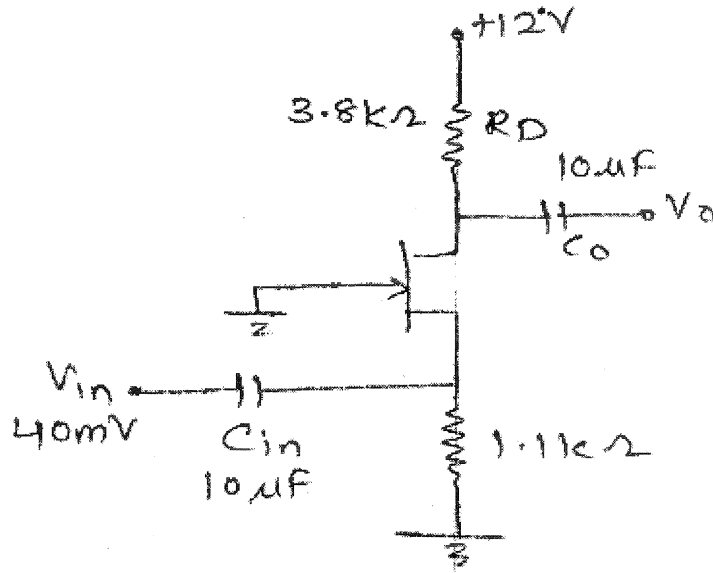6. (a) Calculate Z_{in} , Z_o , A_v and V_o

10

Given : $I_{DSS} = 10\text{mA}$, $V_p = -4\text{V}$, $V_{GSQ} = -2.2\text{V}$



(b) Derive expression for stability for collector to base self bias circuit.

5

(c) Explain characteristics and working of zener diode.

5

[TURN OVER

DBEC DATA SHEET

Transistor type	P_{dmax}	I_{cmax}	$V_{ce}^{(sat)}$	V_{cbo}	V_{ceo}	V_{ces}	V_{ces}	V_{beo}	T_j max	D.C. current gain			Small	Signal	h_{fe}	V_{ce}
	@ 25°C Watts	@ 25°C Amps	volts d.c.	volts d.c.	(Sus) volts d.c.	(Sus) volts d.c.	volts d.c.	volts d.c.		min	typ.	max.	min.	typ.	max.	max.
2N3055	115.5	15.0	1.1	100	60	70	90	7	200	20	50	70	15	50	120	1.8
ECN055	50.0	5.0	1.0	60	50	55	60	5	200	25	50	100	25	75	125	1.5
ECM149	30.0	4.0	1.0	50	40	—	—	8	150	30	50	110	33	60	115	1.2
ECM100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	280	50	90	280	0.9
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	220	125	220	260	0.9
2N525(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	65	—	45	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	450	240	330	500	0.9

Transistor type	h_{ie}	h_{oe}	h_{re}	o_{ja}
BC 147A	2.7 K Ω	18 μ S	1.5×10^{-4}	0.4°C/mw
2N 525 (PNP)	1.4 K Ω	25 μ S	3.2×10^{-4}	—
BC 147B	4.5 K Ω	30 μ S	2×10^{-4}	0.4°C/mw

BFW 11—JFET MUTUAL CHARACTERISTICS

-V _{GS} volts	0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4	2.5	3.0
I _{DS} max. mA	10	9.0	8.3	7.6	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1
I _{DS} typ. mA	7.0	6.0	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0
I _{DS} min. mA	4.0	3.0	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0

N-Channel JFET

Type	V_{DS} max. Volts	V_{DG} max. Volts	V_{GS} max. Volts	P_d max. @25°C	T_j max.	I_{DSS}	g_{m0}	-V _p Volts	r_d	Derate above 25°C
2N3822	50	50	50	300 mW	175°C	2 mA	3000 μ S	6	50 K Ω	2 mW/°C
BFW 11 (typical)	30	30	30	300 mW	200°C	7 mA	5000 μ S	2.5	50 K Ω	—

UJT type	P_d max. @25°C	I_E max. @25°C	I_p peak pulse current max.	V_{B2E} Volts max.	V_{B1E} Volts	T_j max	η min. max.	R_{25} K Ω min. typ.	Max.	I_p max. μ A
2N2646	300mW	50mA	2Amp.	30	35	125°C	0.56 0.75	4.7 7.0	9.1	5.0