

(3 Hours)

(Total Marks: 80)

Please check whether you have the right question paper.

- N.B.:**
- 1) Question number 1 is compulsory and compulsory.
 - 2) Attempt any three questions from the remaining five questions.
 - 3) Figures to the right indicate full marks.

- Q.1** Solve any five questions out of six questions.
- (a) Excess-3 code is called a self-completing code, Justify. [4]
 - (b) State and prove De-Morgan's theorem. [4]
 - (c) Simplify $y = \pi M(1,3,5)$ [4]
 - (d) Explain hazards in combinational circuits. [4]
 - (e) Explain race around condition? [4]
 - (f) Perform following operations using two's complement method: [4]
 - i) $(42)_{10} - (18)_{10}$ ii) $(18)_{10} - (42)_{10}$
- Q.2**
- (a) Implement a full adder using 74138, 3:8 decoder. [10]
 - (b) Explain the operation of J-K Flip Flop using NAND gates. [10]
- Q.3**
- (a) Reduce using Quine McClusky's method: [10]
 - (b) Design a 4 bit binary code to gray code converter. [10]
- Q.4**
- (a) Obtain a 1:32 demultiplexer using four 1:8 demultiplexers and one 1:4 demultiplexer together. [10]
 - (b) Design a MOD 5 asynchronous UP counter using flip-flops. [10]
- Q.5**
- (a) Design a 2 bit magnitude comparator. [10]
 - (b) Design a BCD to seven segment converter with common cathode. [10]
- Q.6** Write short notes on any four of the following: [20]
- (a) Shaft Position Encoding
 - (b) Describe both of the following:
 - i) Standard and Non-Standard SOP form
 - ii) Standard and Non-Standard POS form
 - (c) Bidirectional shift register
 - (d) RTL and DTL Logic families
 - (e) Master-Slave Flip-Flop