

**University of Mumbai**  
**Examination 2020 under cluster 4 (PCE)**

Program: BE Mechanical Engineering  
 Curriculum Scheme: Rev2016  
 Examination: Third Year Semester VI  
 Course Code: MEDLO6021 and Course Name: Mechatronics

Time: 1 hour

Max. Marks: 50


Note to the students:- All the Questions are compulsory and carry equal marks .

Q1.	Which of the following is/are characteristic/s of mechatronic products and systems?
Option A:	No interaction between mechanical, electronic and information technologies
Option B:	Special interaction of subsystems in one physical unit
Option C:	Actuators with electrical auxiliary energy
Option D:	Actuators without electrical auxiliary energy
Q2.	Which control system does not have a stability problem?
Option A:	sequence system
Option B:	electrical system
Option C:	Open loop system
Option D:	Closed loop system
Q3.	In which system does the output not affect the process in any way?
Option A:	Open loop system
Option B:	Closed loop system
Option C:	sequence system
Option D:	pneumatic system
Q4.	Drives are also known as
Option A:	Sensors
Option B:	Actuators
Option C:	Controller
Option D:	Manipulator
Q5.	From the block diagram given in the following figure, the expression of C/R is:
Option A:	$G_1G_2G_3/1-G_2G_1$
Option B:	$G_1G_2/1-G_1G_2G_3$
Option C:	$G_1G_2G_3/1-G_1G_2G_3$
Option D:	$G_1G_2/G_3(1-G_1G_2)$


**University of Mumbai**  
**Examination 2020 under cluster 4 (PCE)**

Q6.	Which material is used to make solenoid core?
Option A:	Copper
Option B:	Silver
Option C:	Iron
Option D:	Aluminum
Q7.	Drones uses
Option A:	Servo motor
Option B:	DC motor
Option C:	Stepper motor
Option D:	BLDC
Q8.	Induction motor required starter because:
Option A:	starting torque is high
Option B:	It's run against heavy load
Option C:	It can not run in reverse direction
Option D:	starting current is more than its rated current
Q9.	A reading is recorded as 23.90 Centigrade. The reading has
Option A:	three significant figures
Option B:	four significant figures
Option C:	two significant figures
Option D:	five significant figures
Q10.	<b>The mechatronics is an interdisciplinary field in which the disciplines those act together are _____</b>
Option A:	Mechanical systems and Electronic systems
Option B:	Mechanical systems and Information technology
Option C:	Electronic systems and Information technology
Option D:	Mechanical systems, Electronic systems and Information technology
Q11.	<b>On-off Control is also called as _____.</b>
Option A:	one position control
Option B:	two position control
Option C:	four position control
Option D:	half position control
Q12.	<b>The capability of convention relay systems for complex operations is _____ that of the PLCs .</b>
Option A:	poor than
Option B:	excellent than
Option C:	as good as
Option D:	unpredictable as
Q13.	<b>Heat in thermal system is analogous to _____ in electrical energy.</b>
Option A:	Current
Option B:	potential difference
Option C:	Resistance

**University of Mumbai**  
**Examination 2020 under cluster 4 (PCE)**

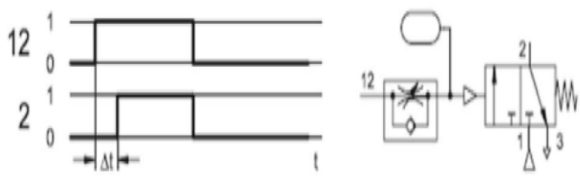Option D:	Charge
Q14.	What is the function of sequence valve used in hydraulic circuits?
Option A:	sequence valves are used to perform number of operations one after the other after the set pressure is reached
Option B:	sequence valves are used to perform number of operations continuously before the set pressure is reached
Option C:	sequence valves after reaching set pressure oil is flown to the tank
Option D:	no use
Q15.	Which of the following is applicable for bleed off circuits?
Option A:	bleed off circuits develop heat in the system
Option B:	bleed off circuits are used for resistive loads
Option C:	bleed off circuits are used for runaway loads
Option D:	no use
Q16.	Why the pilot operated check valve used in clamping operation?
Option A:	To reduce leakage in spool valve and to avoid decrease in pressure during clamping
Option B:	To increase pressure during clamping
Option C:	To filter the pumped oil
Option D:	Not used in clamping
Q17.	The valve symbol shown in the figure is 
Option A:	ON delay (Normally close) valve
Option B:	OFF delay (Normally open) valve
Option C:	Pressure relief valve
Option D:	Sequence valve
Q18.	If a pole is located at origin, how does it get represented on the magnitude plot
Option A:	$-10 \log (\omega) \text{ dB}$
Option B:	$-20 \log (\omega) \text{ dB}$
Option C:	$-40 \log (\omega) \text{ dB}$
Option D:	$-60 \log (\omega) \text{ dB}$
Q19.	At which condition of ' $\xi$ ', resonant peak does not exist and its maximum value is considered to be unity along with zero resonant frequency
Option A:	$0 < \xi < 0.707$
Option B:	$\xi > 0.707$
Option C:	$\xi = 0$

**University of Mumbai**  
**Examination 2020 under cluster 4 (PCE)**

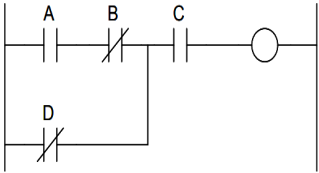Option D:	$\xi = 1$
Q20.	Angle of Asymptotes in Open loop Transfer function, as given below, by Root locus method are  $G(S)H(S) = \frac{K}{S(S+6)(S^2+4S+13)}$
Option A:	$60^\circ, 180^\circ, 300^\circ$
Option B:	$40^\circ, 80^\circ, 120^\circ, 160^\circ$
Option C:	$45^\circ, 135^\circ, 225^\circ, 315^\circ$
Option D:	$80^\circ, 160^\circ, 240^\circ, 320^\circ$
Q21.	Proportional band of a controller is expressed as
Option A:	Percentage
Option B:	Range of control variable
Option C:	Ratio
Option D:	Gain
Q22.	The boolean representation of the given PLC program is  
Option A:	$ABC + D$
Option B:	$C + D(A+B)$
Option C:	$C(AB + D)$
Option D:	$ABC + BD$
Q23.	Why latches are called memory devices?
Option A:	It has capability to store 8 bits of data
Option B:	It has internal memory of 4 bits
Option C:	It can store 1 bit of data
Option D:	It can store infinite amount of data
Q24.	In PLC, scan time refers to the amount of time in which
Option A:	timer and counters are indexed by
Option B:	one rung of ladder logic takes to get complete
Option C:	the entire program takes to execute
Option D:	the technician enters the program
Q25.	Latch is a device with
Option A:	One stable state

**University of Mumbai**  
**Examination 2020 under cluster 4 (PCE)**

Option B:	Two stable states
Option C:	Three stable states
Option D:	Infinite stable states

**University of Mumbai**  
**Examination 2020 under cluster 4 (PCE)**

Program: BE Mechanical Engineering

Curriculum Scheme: Rev2016

Examination: Third Year Semester VI

Course Code: MEDLO6021 and Course Name: Mechatronics

Time: 1 hour

Max. Marks: 50

---

---

<b>Question</b>	<b>Correct Option (Enter either 'A' or 'B' or 'C' or 'D')</b>
Q1.	B
Q2.	C
Q3.	A
Q4	B
Q5	A
Q6	C
Q7	D
Q8.	D
Q9.	B
Q10.	D
Q11.	B
Q12.	A
Q13.	D
Q14.	A
Q15.	C
Q16.	A
Q17.	A
Q18.	B
Q19.	B
Q20.	C
Q21.	A
Q22.	C
Q23.	C
Q24.	C
Q25.	B